

ELCT 201 – EE LABORATORY

PROJECT ZERO: INSTRUMENT SKILLS

KAILEN KING

1/26/2022

DEPARTMENT OF ELECTRICAL ENGINEERING
UNIVERSITY OF SOUTH CAROLINA
COLUMBIA, SC 29208

ABSTRACT

A set of exercises taught basic use of the oscilloscope, function generator, and digital multimeter. The oscilloscope trigger controls were found to be especially important for capturing the interesting parts of a voltage waveform, while the voltage and time (vertical and horizontal) controls were important for displaying the interesting features at a size that was appropriate to see and measure. The function generator could produce several different waveforms including sine, triangle, and pulse, with user-selected properties such as frequency and amplitude, and also several option parameters such as duty, and dc offset. Importantly, the function generator was not an ideal voltage source, but instead had a 50Ω output resistance. The digital multimeter turned out to be a good tool for quickly measuring the rms value of a signal, or the dc offset of a signal.

INTRODUCTION

A resistive voltage divider, as shown in Figure 1 served as the circuit foil for learning to use the bench instruments.

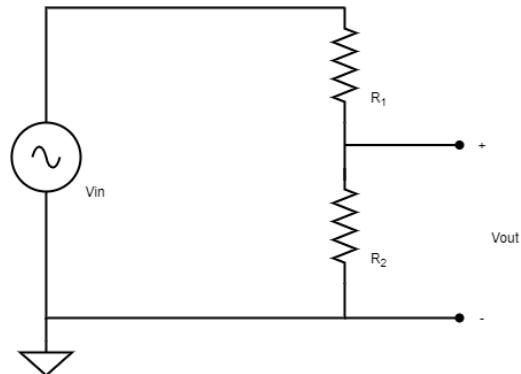


Figure 1 Resistive voltage divider circuit.

The circuit has a frequency-independent transfer function, V_{out}/V_{in} , given as:

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2} \quad (\text{Eq 1})$$

For equal values of R_1 and R_2 , regardless of the actual value of resistance, the voltage transfer function always equals 0.5; the open-circuit (unloaded) output voltage is always $\frac{1}{2}$ of the input voltage.

MEASURING VARIOUS WAVEFORMS

The function generator was set to deliver several different waveforms and the oscilloscope controls were set to display the important features of these waveforms. The following figures illustrate the measurements that were made.

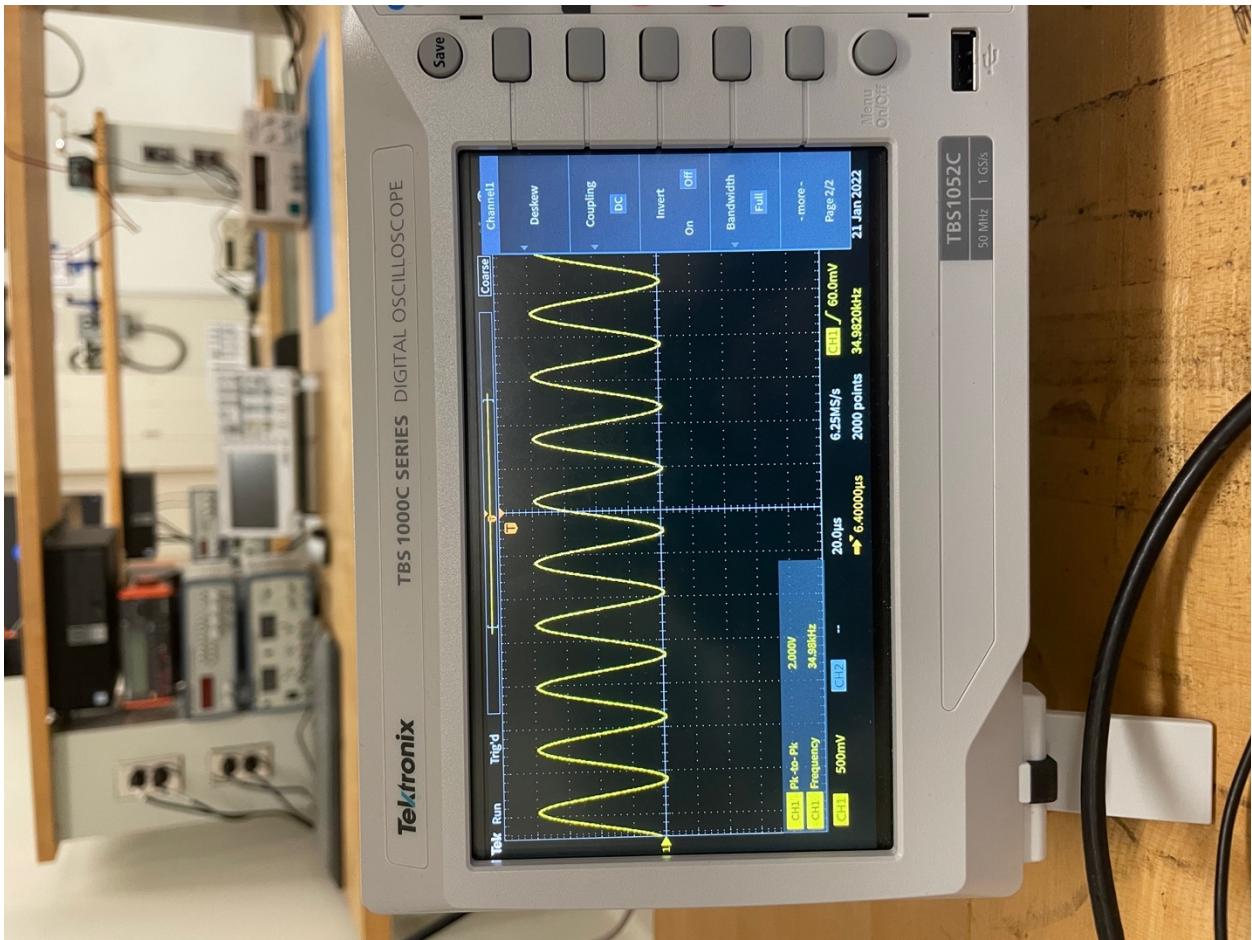


Figure 2. Oscilloscope screen showing function generator delivering a sine wave at 35 kHz, 2Vpp, with +1V dc offset.

your pictures are hard to read, please try to use a memory stick or edit them in a better form

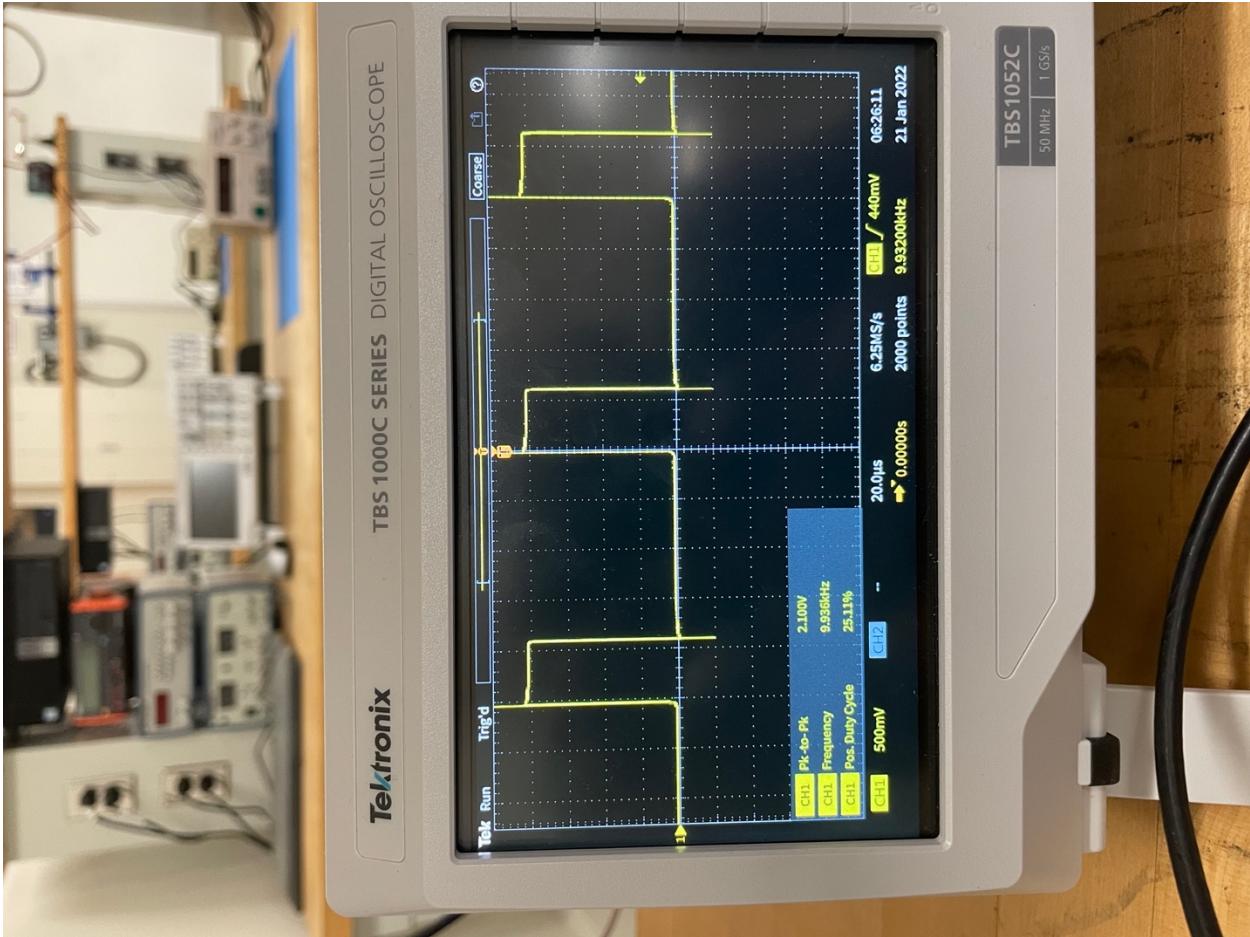


Figure 3. Oscilloscope screen showing a pulse wave having pulse frequency of 10 kHz, low level 0 V, high level 4 V, pulse duty of 25%.

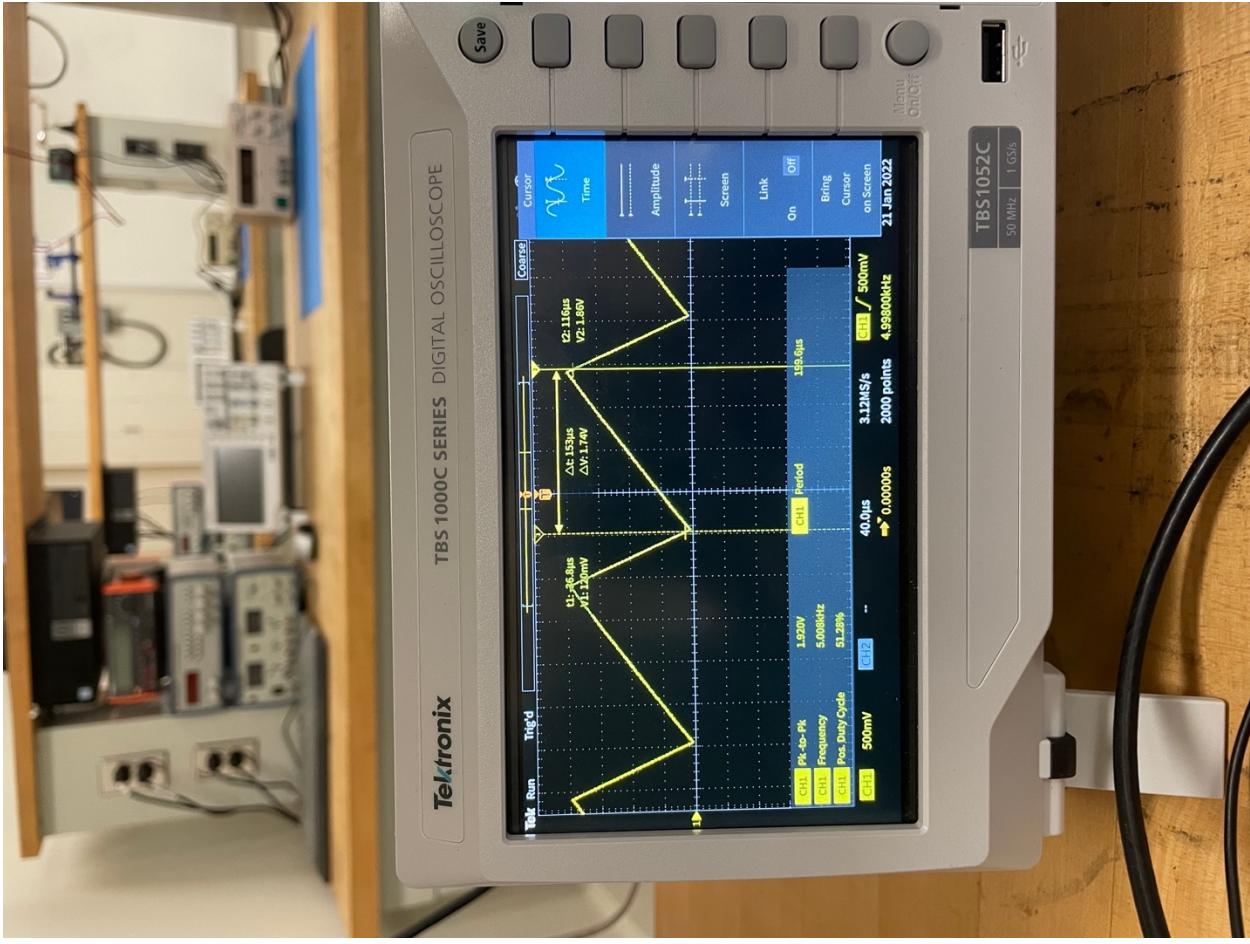


Figure 4. Oscilloscope screen showing a triangle wave having period of 200 μ s, lowest voltage 0 V, highest voltage 4 V, ramp up time 75% of period, ramp-down time 25% of period.

COMPARING OSCILLOSCOPE AND MULTIMETER MEASUREMENTS

The voltage divider was set up with two $1000\ \Omega$ resistors, then the function generator was set to produce an open-circuit voltage of $2\ V_{pp}$ at 10 kHz. The oscilloscope was set to trigger on the rising edge of the channel 1 waveform at a trigger level of $+0.5V$ to produce the waveform shown in Figure 5.

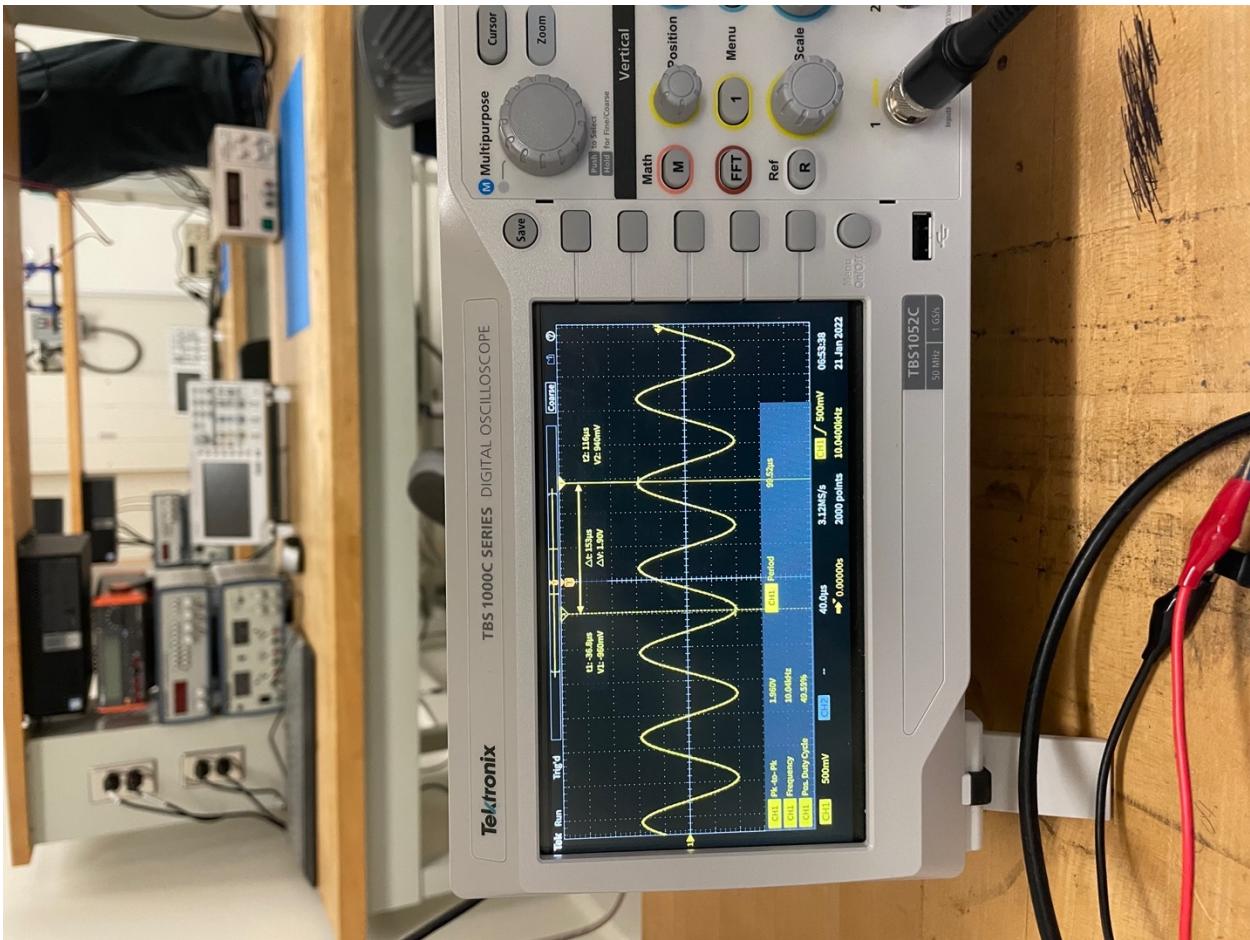


Figure 5. Waveform for which the voltage equation of time was computed.

The equation of this voltage waveform is

$$V(t) = V \sin \omega t \quad \text{you need to write the values in this equation} \quad \text{Equation 1}$$


After connecting the function generator to the input terminals of the voltage divider, the input and output voltages were measured on Ch 1 and Ch 2 respectively, of the oscilloscope. The results are shown in Figure 6.




Insert figure

Figure 6. Oscilloscope screen showing simultaneous measurement of the input and output voltages of the voltage divider circuit.

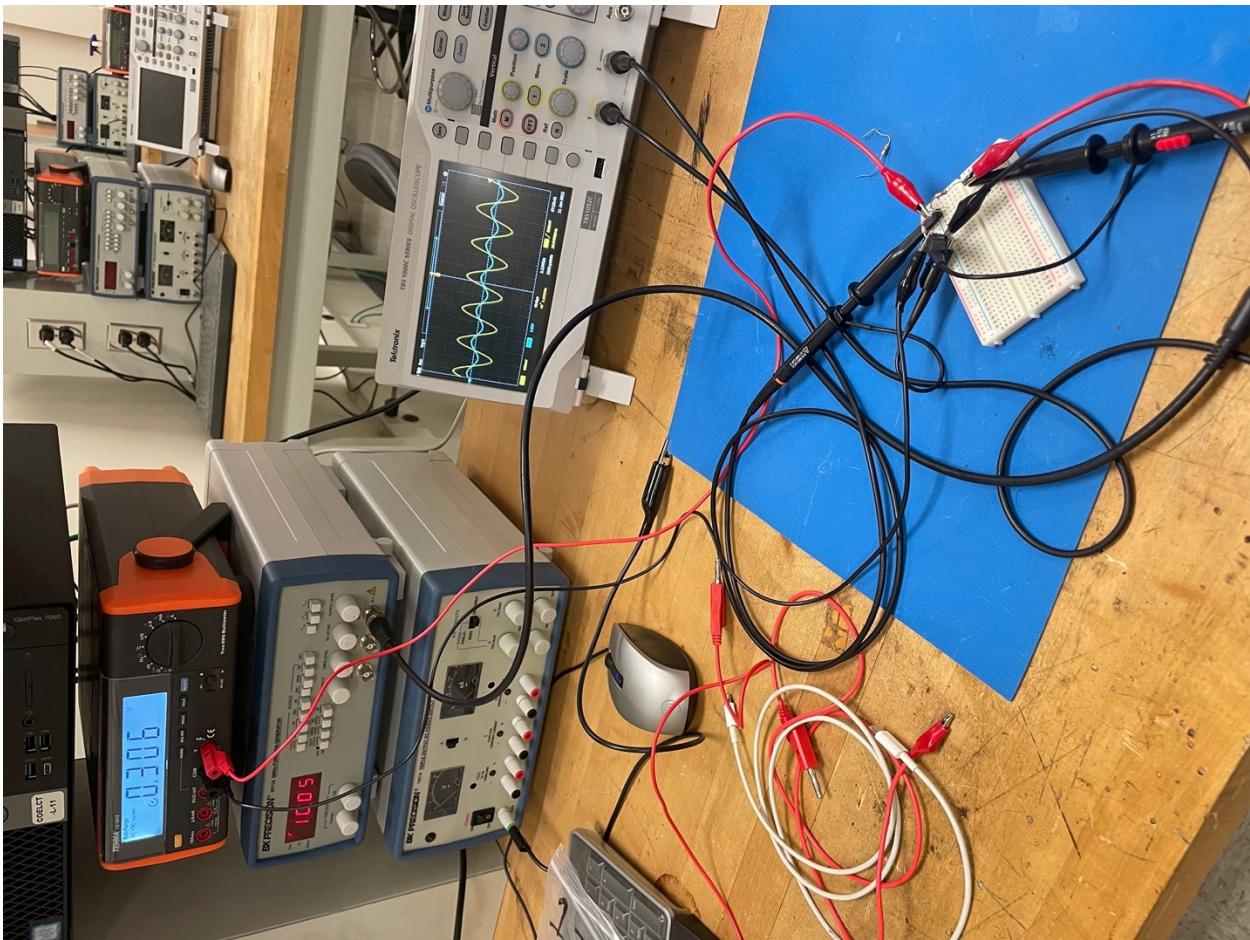The rms values of the input and output voltages were then measured with the digital multimeter and found to agree with the oscilloscope measurements based on the attached screenshots. (That is, when the rms values were multiplied by $\sqrt{2}$ to compute the peak amplitude of the sine wave, that peak amplitude was equal to the value measured by the oscilloscope.



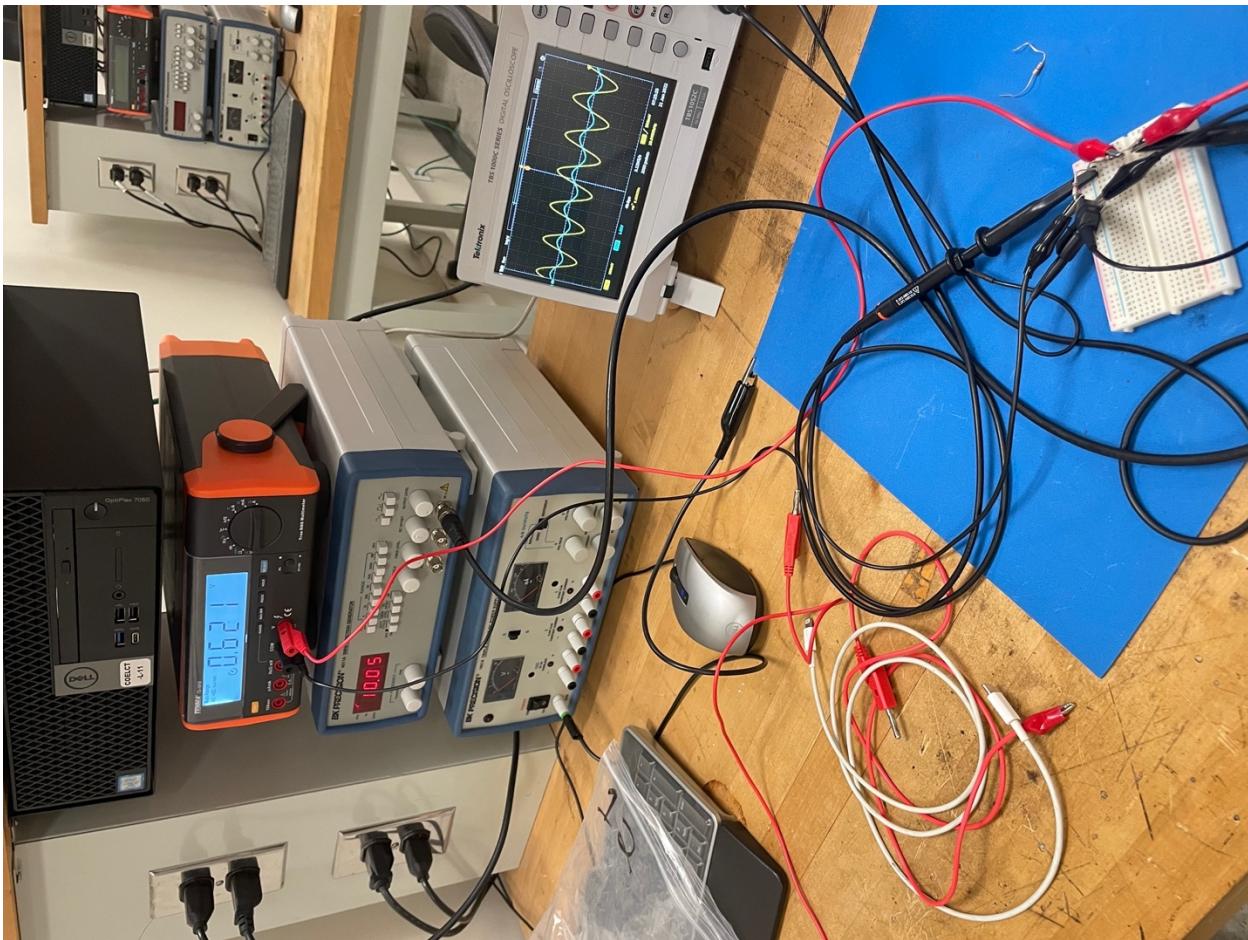

LOADING EFFECT ON FUNCTION GENERATOR

In a final experiment, the resistive voltage divider was rebuilt using two $50\ \Omega$ resistors. When the function generator was reconnected, without changing the voltage amplitude knobs, both the input and output voltages were observed to be lower than in the previous measurement where the voltage divider was constructed from two $1000\ \Omega$ resistors. The reason is because the resistors were connected in series when the resistance is reduced the voltage decreases.

the reason is because of the values of the resistors

This happened because the resistance was significantly reduced.

CONCLUSIONS

This project was very useful for introducing the basic controls of the three benchtop instruments. A significant finding is that the function generator does not act like an ideal voltage source, but instead it acts like a voltage source behind a $50\ \Omega$ resistance. This has a result that the voltage applied to a circuit will be slightly different, or maybe even significantly different, than open circuit voltage, so loading effects should always be considered.